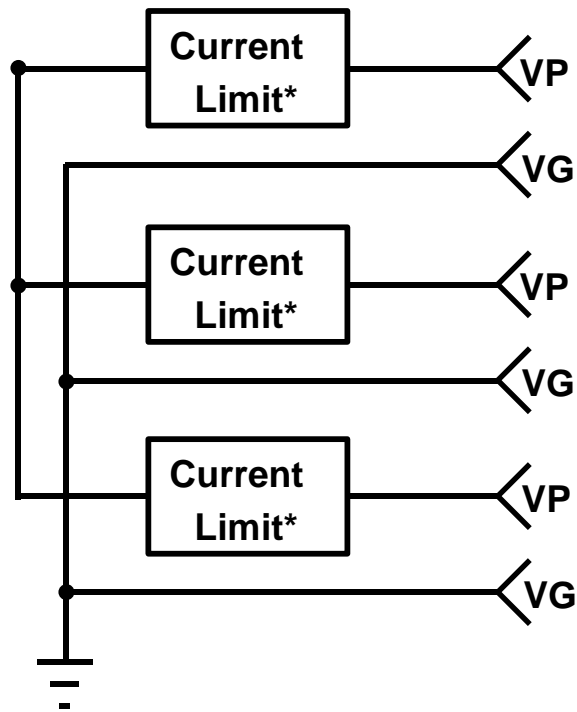


Agency Requirements for Power Distribution on 1394

David R. Wooten
Compaq Computer Corp.

- According to IEC950, ‘inherently limited’ supplies must limit output current on user accessible connections wire to 8A if voltage $< 20V$ and to 100 VA if voltage $> 20V$
- UL requires that protection must limit short circuit current to less than 8A within 60 sec.
- For supplies that are not ‘inherently limited’ limit is 5A if voltage $< 20V$ and 100VA if voltage > 20 .




***Pass 1.5A, trip at 3.0A**

Self powered node

Rules for self powered node

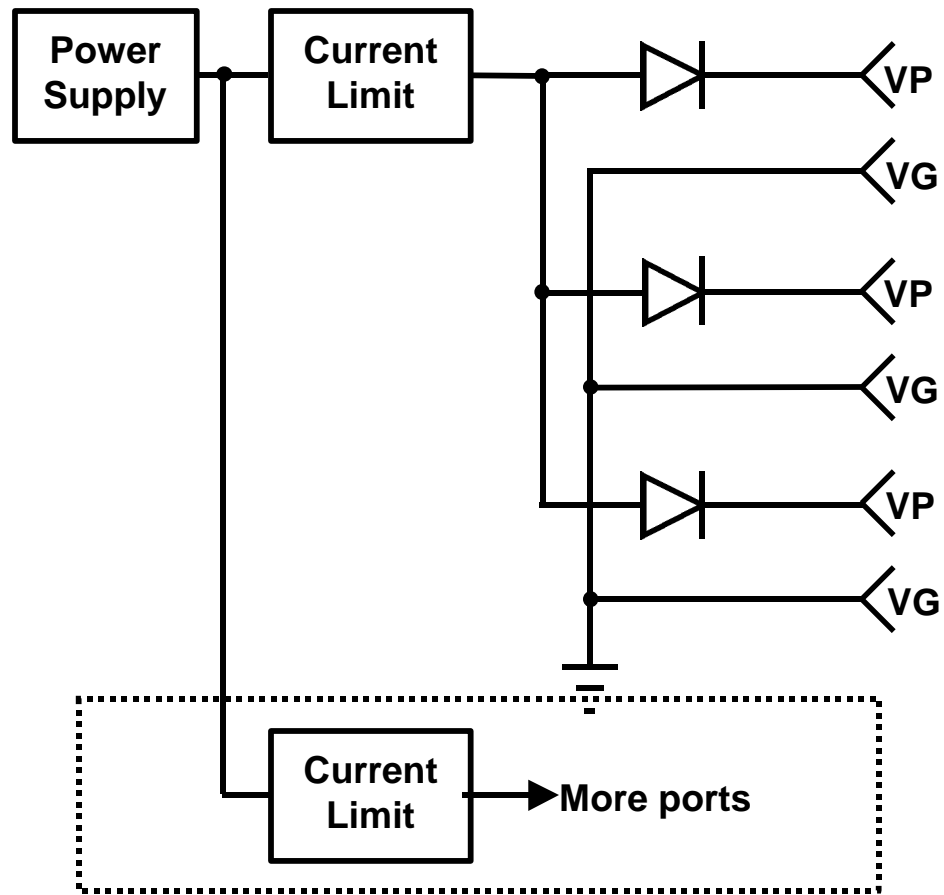
- Self powered node than can sum two power sources into a third output must have current limiting on each port
- Easiest current limiting is poly fuse that will pass 1.5A and trip at 3.0A



Power supply with diode per port

Rules for supply with diode per port

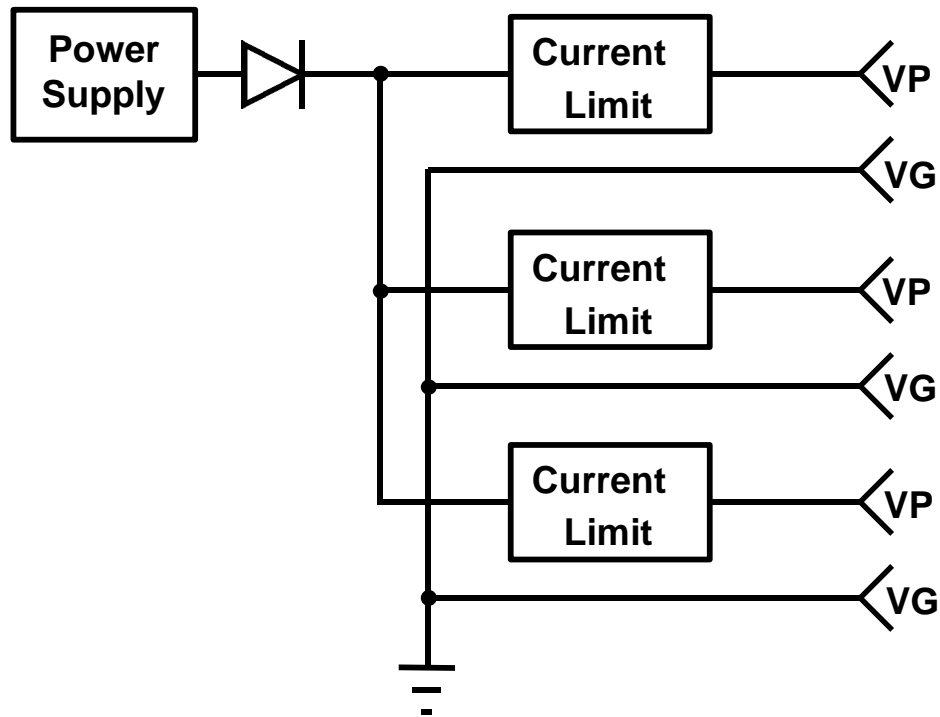- Maximum current out any node must be $< 8A$ or $100 VA$
- Examples
 - If supply is $20V$ and $1.5A$ per port, then have up to 3 ports on each current limiting device (as shown on previous foil.)
 - If supply is $12V$ and $1.5A$ per port, then can have 5 ports on each current limiting device.



Supply with single diode isolation

Rules for supply with single diode isolation

- If only one port, then only need single current limiting device
- If more than two ports, then need current limiting device on each port
 - Because the node is also providing power, this is equivalent to three node, self powered device