



500 Volt Capacitive Isolation Barriers

-December '97 P1394a/b meetings-



LAN versus SCSI?

◆ SCSI/Parallel/Serial Port

- Short cable runs, local peripherals only
- Copper shields tie directly to the PC bulkhead
- Same Green Wire ground assumption
- Ground loops, galvanic isolation are ignored

◆ LAN's


- Long cable runs, daisy chains of boxes, distant peripherals
- Green Wire grounds are uncontrolled
- Full galvanic isolation for fire and shock hazard elimination
 - » 500 Volts isolation barrier required
 - » Double fault protection, i.e., no single component failure hazards the box

◆ 1394a/b

- LAN or SCSI?
- This is a “religious” issue




IEEE 1394-1995 Example Barrier

 



Capacitor Modeling

 

Inductance – Inductance is simply a function of path length and aspect ratio. A 1206 package measures around 1200pH regardless of capacitance, voltage rating and dielectric.

$$R_{Series} = R_{ESR-resonance} \left(1 + 10^{(|\log(f / f_{res})| - x)} \right)$$


$x \sim 1.6 \text{ to } 1.8$

Equivalent Series Resistance	Capacitance	Max. Volt	Resonant Freq.	Inductance
500 mOhms	1000 pf	500 Volts	145 MHz	1200 pH
300	2200	500	98	1200
850	2200	50	98	1200

(Data for capacitor part: 12067C102MAT2A)



Equivalent Series Resistance


 


$$R_{Series} = R_{ESR-resonance} \left(1 + 10^{(|\log(f / f_{res})| - x)} \right)$$

$x \sim 1.6 \text{ to } 1.8$



Realistic Capacitive Barrier

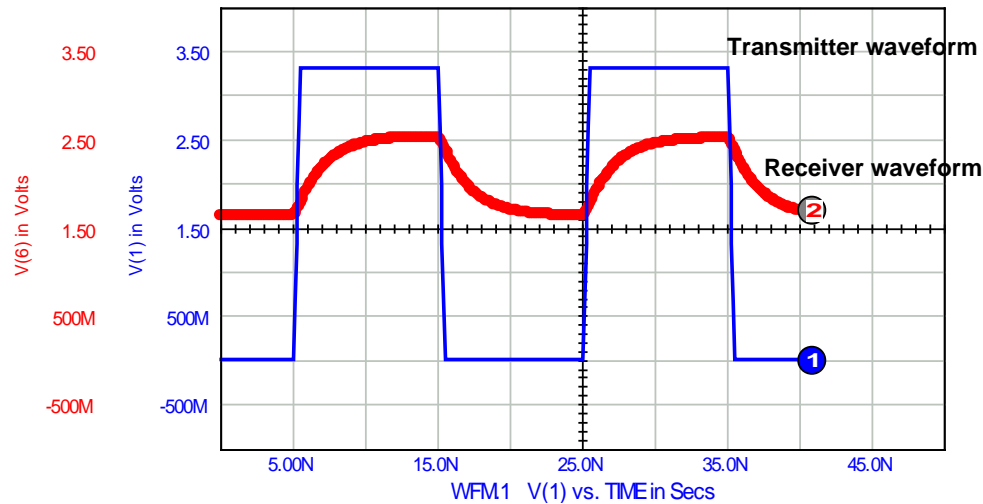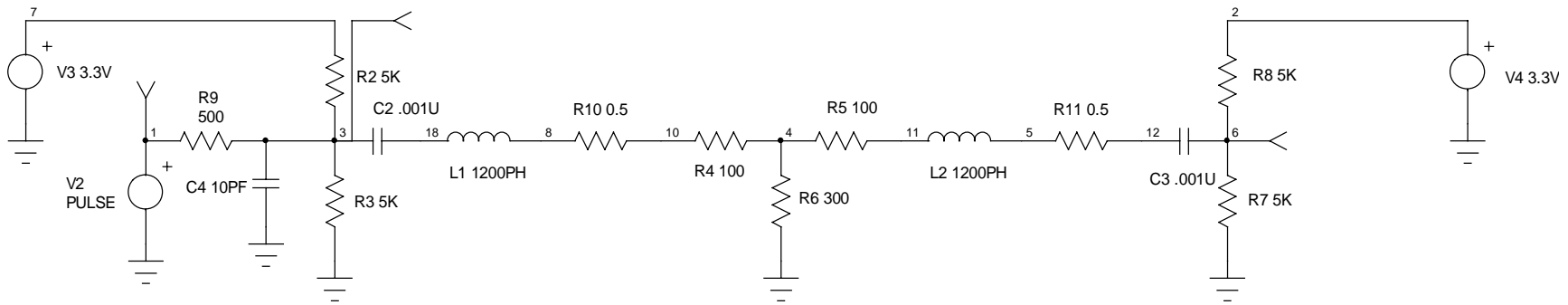

Spice Simulation



Capacitive Barrier Comments

- ◆ **We see the ~2 ns delay time in propagating signals across the isolation barrier.**
 - The source of this delay time is not, however, the isolation barrier. To create a finite delay time it was necessary to “soften” the signal source’s waveform with an RC circuit. 500 Ohms and 10 pF were chosen to reproduce TI’s data sheet pin specifications for test loads and maximum output current.
 - An ideal waveform would cross the isolation barrier with no delay time. Perhaps the mere physical presence of the circuit elements, e.g., the capacitors and resistance networks, add enough capacitance to ground to account for this observation in real systems.

- ◆ **The isolation barrier’s internal time constants are irrelevant for delay times.**
 - RC ~ 100 ns and L/R ~ 10 ps.
 - Since the capacitor’s self-resonance frequency is around 100 MHz and our logic signals change on a 20 ns time scale we see that actual capacitors in the barrier circuit act as inductors for the high frequency components of the logic signals.

- ◆ **In any case it is clear that using high voltage capacitors (and even doubling them up in series for double fault protection) will have no tangible effect on PHY to LINK signaling.**